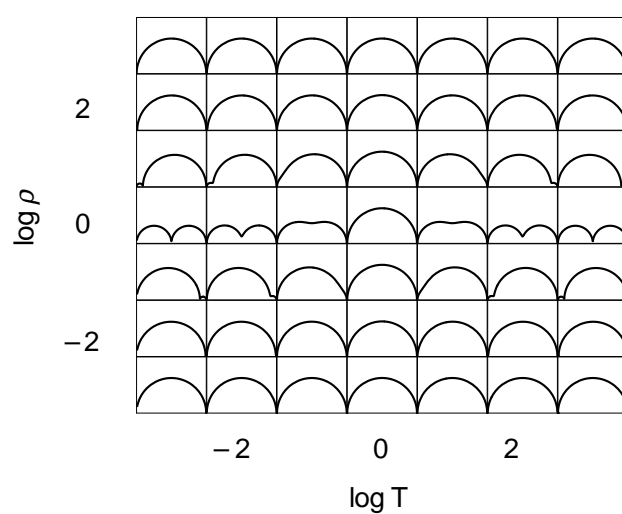


Handbook of Electrochemical Impedance Spectroscopy



CIRCUITS made of RESISTORS and CAPACITORS

ER@SE/LEPMI

J.-P. Diard, B. Le Gorrec, C. Montella

Hosted by Bio-Logic @ www.bio-logic.info



September 10, 2007

Contents

1	Circuits made of one R and one C	5
1.1	Circuit $(R+C)$	5
1.1.1	Impedance	5
1.1.2	Reduced impedance	5
1.2	Circuit (R/C)	5
1.2.1	Impedance	6
1.2.2	Reduced impedance	6
2	Circuits made of two Rs and one C	7
2.1	Circuit $(R_2+(R_1/C_1))$	7
2.1.1	Impedance	7
2.1.2	Reduced impedance	7
2.2	Circuit $((R_1+C_1)/R_2)$	8
2.2.1	Impedance	8
2.2.2	Reduced impedance	8
2.3	Transformation formulae between $(R+(R/C))$ and $((R+C)/R)$ circuits	8
2.3.1	Transformation formulae $(R+(R/C)) \rightarrow ((R+C)/R)$. . .	8
2.3.2	Transformation formulae $((R+C)/R) \rightarrow (R+(R/C))$. . .	9
3	Circuits made of one R and two Cs	11
3.1	Circuit $((R_1/C_1)+C_2)$	11
3.1.1	Impedance	11
3.1.2	Reduced impedance	11
3.2	Circuit $((R_1+C_2)/C_1)$	12
3.2.1	Impedance	12
3.2.2	Reduced impedance	13
3.3	Transformation formulae between $((R/C)/C)$ and $((R+C)/C)$ circuits	13
3.3.1	Transformation formulae $((R/C)/C) \rightarrow ((R+C)/C)$. . .	13
3.3.2	Transformation formulae $((R+C)/C) \rightarrow ((R/C)/C)$. . .	14
4	Circuits made of two Rs and two Cs	15
4.1	Circuit $((R_1/C_1)+(R_2/C_2))$	15
4.1.1	Impedance	15
4.1.2	Reduced impedance	15
4.2	Circuit $((R_1+(R_2/C_2))/C_1)$	18
4.2.1	Impedance	18

4.2.2	Reduced impedance	18
4.3	Circuit $((C_1+(R_2/C_2))/R_1)$	21
4.3.1	Impedance	21
4.3.2	Reduced impedance	21
4.4	Circuit $((C_2+R_2)/R_1)/C_1)$	23
4.4.1	Impedance	23
4.4.2	Reduced impedance	23
4.5	Transformation formulae for RRCC circuits	25
4.5.1	Transformation formulae circuit 2 \rightarrow circuit 1	25
4.5.2	Transformation formulae circuit 1 \rightarrow circuit 2	26
4.5.3	Transformation formulae circuit 3 \rightarrow circuit 1	26
4.5.4	Transformation formulae circuit 1 \rightarrow circuit 3	27
4.5.5	Transformation formulae circuit 4 \rightarrow circuit 1	27
4.5.6	Transformation formulae circuit 1 \rightarrow circuit 4	27
4.5.7	Transformation formulae circuit 3 \rightarrow circuit 2	27
4.5.8	Transformation formulae circuit 2 \rightarrow circuit 3	28
4.5.9	Transformation formulae circuit 4 \rightarrow circuit 2	28
4.5.10	Transformation formulae circuit 2 \rightarrow circuit 4	28
4.5.11	Transformation formulae circuit 4 \rightarrow circuit 3	28
4.5.12	Transformation formulae circuit 3 \rightarrow circuit 4	28

Chapter 1

Circuits made of one R and one C

1.1 Circuit (R+C)

The symbol '+' denotes the serial association of electrical components.

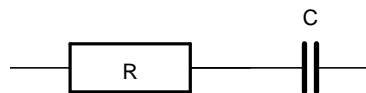


Figure 1.1: Circuit (R+C).

1.1.1 Impedance

$$Z(\omega) = R + \frac{1}{C i \omega} = \frac{R(1 + i \omega \tau)}{i \omega \tau}, \quad \tau = RC$$

$$\operatorname{Re} Z(\omega) = R, \quad \operatorname{Im} Z(\omega) = -\frac{R}{\tau \omega}$$

1.1.2 Reduced impedance

$$Z^*(u) = Z/R = 1 + \frac{1}{i u} = \frac{1 + i u}{i u}, \quad u = \tau \omega, \quad \operatorname{Re} Z^*(u) = 1, \quad \operatorname{Im} Z^*(u) = -\frac{1}{u} \quad (1.1)$$

(Fig. 1.2)

1.2 Circuit (R/C)

The symbol '/' denotes the parallel association of electrical components.

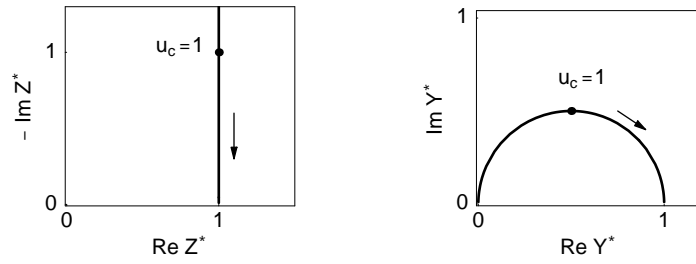


Figure 1.2: Nyquist diagram of the reduced impedance and admittance ($Y^* = RY$) for the (R+C) circuit (Fig. 1.1, Eq. (1.1)). The arrows always indicate the increasing frequency direction.

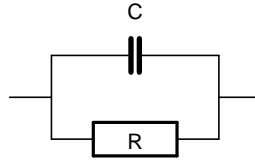


Figure 1.3: Circuit (R/C).

1.2.1 Impedance

$$Z(\omega) = \frac{R}{1 + i\omega\tau}, \quad \tau = RC$$

$$\operatorname{Re} Z(\omega) = \frac{R}{1 + \tau^2\omega^2}, \quad \operatorname{Im} Z(\omega) = -\frac{R\tau\omega}{1 + \tau^2\omega^2}$$

1.2.2 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R} = \frac{1}{1 + iu}, \quad u = \tau\omega, \quad \operatorname{Re} Z^*(u) = \frac{1}{1 + u^2}, \quad \operatorname{Im} Z^*(u) = -\frac{u}{1 + u^2} \quad (1.2)$$

(Fig. 1.4)

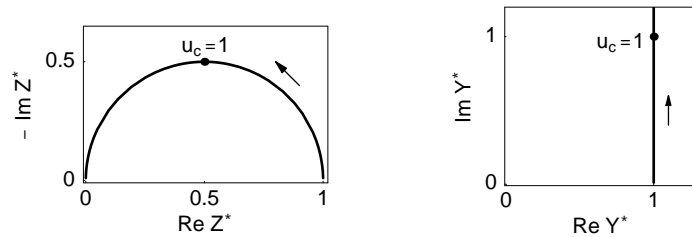


Figure 1.4: Nyquist diagram of the reduced impedance and admittance ($Y^* = RY$) for the (R/C) circuit (Fig. 1.3, Eq. (1.2)).

Chapter 2

Circuits made of two Rs and one C

2.1 Circuit ($R_2 + (R_1/C_1)$)

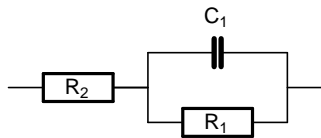


Figure 2.1: Circuit ($R_2 + (R_1/C_1)$).

2.1.1 Impedance

$$Z(\omega) = R_2 + \frac{1}{i\omega C_1 + \frac{1}{R_1}}$$

$$Z(\omega) = \frac{(R_1 + R_2)(1 + i\omega\tau_2)}{1 + i\omega\tau_1}, \quad \tau_1 = R_1 C_1, \quad \tau_2 = \frac{C_1 R_1 R_2}{R_1 + R_2}$$

2.1.2 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R_1 + R_2} = \frac{1 + T i u}{1 + i u} \tag{2.1}$$

$$u = \tau_1 \omega, \quad T = \tau_2 / \tau_1 = R_2 / (R_1 + R_2) < 1$$

$$\operatorname{Re} Z^*(u) = \frac{1 + T u^2}{1 + u^2}, \quad \operatorname{Im} Z^*(u) = \frac{(T - 1) u}{1 + u^2}$$

$$\lim_{u \rightarrow 0} \operatorname{Re} Z^*(u) = 1, \quad \lim_{u \rightarrow \infty} \operatorname{Re} Z^*(u) = T$$

(Fig. 2.2)

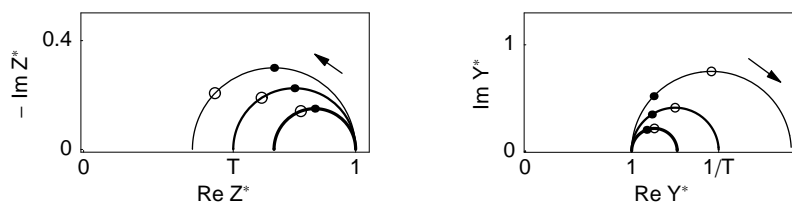


Figure 2.2: Nyquist diagram of the reduced impedance and admittance ($Y^* = (R_1 + R_2)Y$) for the $(R_2 + (R_1/C_1))$ circuit (Fig. 2.1, Eq. (2.1)) with $T = 0.4, 0.55, 0.7$. The line thickness increases with increasing T). Dots: reduced characteristic angular frequency $u_{c1} = 1$; circles: reduced characteristic angular frequency $u_{c2} = 1/T$.

2.2 Circuit $((R_1 + C_1)/R_2)$

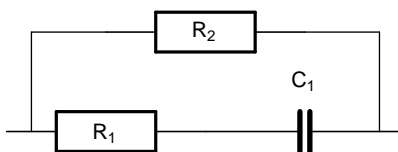


Figure 2.3: Circuit $((R_1 + C_1)/R_2)$.

2.2.1 Impedance

$$Z(\omega) = \frac{R_2 (1 + i\omega \tau_2)}{1 + i\omega \tau_1}, \quad \tau_1 = C_1 (R_1 + R_2), \quad \tau_2 = R_1 C_1$$

$$\operatorname{Re} Z(\omega) = \frac{R_2 (1 + \omega^2 \tau_1 \tau_2)}{1 + \omega^2 \tau_1^2}, \quad \operatorname{Im} Z(\omega) = \frac{\omega R_2 (-\tau_1 + \tau_2)}{1 + \omega^2 \tau_1^2}$$

2.2.2 Reduced impedance

$$Z^*(u) = Z(u)/R_2 = \frac{1 + T i u}{1 + i u} \quad (2.2)$$

$$u = \tau_1 \omega, \quad T = \tau_2/\tau_1 = R_1/(R_1 + R_2) < 1$$

cf. Eq. (2.1) and Fig. 2.2.

2.3 Transformation formulae between $(R + (R/C))$ and $((R + C)/R)$ circuits

2.3.1 Transformation formulae $(R + (R/C)) \rightarrow ((R + C)/R)$

$$R_{22} = R_{11} + R_{21}, \quad R_{12} = R_{11} + \frac{R_{11}^2}{R_{21}}, \quad C_{12} = \frac{C_{11} R_{21}^2}{(R_{11} + R_{21})^2}$$

2.3. TRANSFORMATION FORMULAE BETWEEN $(R+(R/C))$ AND $((R+C)/R)$ CIRCUITS 9

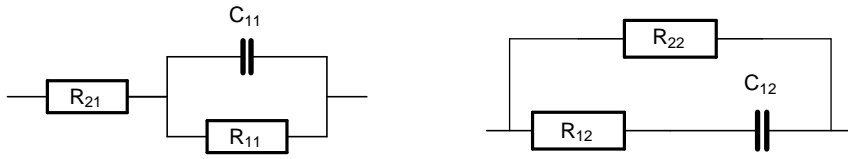


Figure 2.4: The $(R+(R/C))$ and $((R+C)/R)$ circuits are non-distinguishable [3, 2, 1, 6].

2.3.2 Transformation formulae $((R+C)/R) \rightarrow (R+(R/C))$

$$C_{11} = \frac{C_{12} (R_{12} + R_{22})^2}{R_{22}^2}, R_{11} = \frac{R_{12} R_{22}}{R_{12} + R_{22}}, R_{21} = \frac{R_{22}^2}{R_{12} + R_{22}}$$

Chapter 3

Circuits made of one R and two Cs

3.1 Circuit $((R_1/C_1)+C_2)$

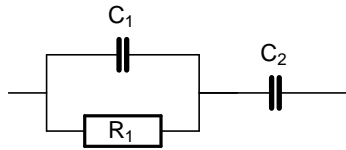


Figure 3.1: Circuit $((R_1/C_1)+C_2)$.

3.1.1 Impedance

$$Z(\omega) = \frac{1}{i\omega C_1 + \frac{1}{R_1}} + \frac{1}{i\omega C_2} = \frac{1 + i\omega (C_1 + C_2) R_1}{i\omega C_2 (1 + i\omega C_1 R_1)}$$

$$Z(\omega) = \frac{1 + i\omega \tau_2}{i\omega C_2 (1 + i\omega \tau_1)}, \quad \tau_1 = R_1 C_1, \quad \tau_2 = (C_1 + C_2) R_1, \quad \tau_1 < \tau_2$$

$$\operatorname{Re} Z(\omega) = -\frac{\tau_1 - \tau_2}{C_2 (1 + \omega^2 \tau_1^2)}, \quad \operatorname{Im} Z(\omega) = -\frac{1 + \omega^2 \tau_1 \tau_2}{\omega C_2 (1 + \omega^2 \tau_1^2)}$$

$$\lim_{\omega \rightarrow 0} \operatorname{Re} Z(\omega) = R_1$$

3.1.2 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R_1} = \frac{1}{T - 1} \frac{1 + T i u}{i u (1 + i u)} \quad (3.1)$$

$$u = \omega \tau_1, \quad T = \tau_2/\tau_1 = 1 + C_2/C_1 > 1$$

$$\operatorname{Re} Z^*(u) = \frac{1}{1+u^2}, \quad \operatorname{Im} Z^*(u) = -\frac{1+u^2 T}{(T-1)u(1+u^2)}$$

$$\lim_{u \rightarrow 0} \operatorname{Re} Z^*(u) = 1$$

(Fig. 3.2)

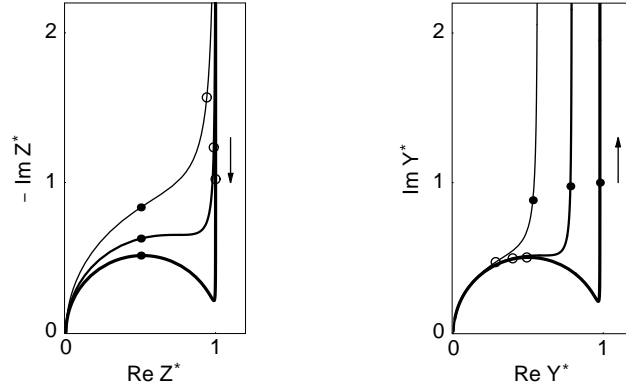
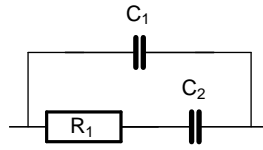


Figure 3.2: Nyquist diagram of the reduced impedance and admittance ($Y^* = R_1 Y$) for the $((R_1/C_1)+C_2)$ circuit (Fig. 3.1, Eq. (3.1)) plotted for $T = 4, 9, 90$. The line thickness increases with increasing T . Horizontal tangent is observed for $T \geq 9$ ($C_2/C_1 \geq 8$) [4]. Dots: reduced characteristic angular frequency $u_{c1} = 1$; circles: reduced characteristic angular frequency $u_{c2} = 1/T$.

3.2 Circuit $((R_1+C_2)/C_1)$

Figure 3.3: Circuit $((R_1+C_2)/C_1)$.

3.2.1 Impedance

$$Z(\omega) = \frac{1}{i\omega C_1 + \frac{1}{R_1 + \frac{1}{i\omega C_2}}} = \frac{1 + i\omega C_2 R_1}{i\omega (C_1 + C_2) \left(1 + \frac{i\omega C_1 C_2 R_1}{C_1 + C_2}\right)}$$

$$Z(\omega) = \frac{(1 + i\omega \tau_2)}{i\omega (C_1 + C_2) (1 + i\omega \tau_1)}, \quad \tau_1 = \frac{C_1 C_2 R_1}{C_1 + C_2}, \quad \tau_2 = C_2 R_1 \quad (3.2)$$

3.3. TRANSFORMATION FORMULAE BETWEEN $((R/C)/C)$ AND $((R+C)/C)$ CIRCUITS 13

$$\operatorname{Re} Z(\omega) = \frac{-\tau_1 + \tau_2}{(C_1 + C_2)(1 + \omega^2 \tau_1^2)}, \quad \operatorname{Im} Z(\omega) = -\frac{1 + \omega^2 \tau_1 \tau_2}{\omega (C_1 + C_2)(1 + \omega^2 \tau_1^2)}$$

$$\lim_{\omega \rightarrow 0} \operatorname{Re} Z(\omega) = \frac{C_2^2 R_1}{(C_1 + C_2)^2}$$

3.2.2 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R_1} = \frac{T-1}{T^2} \frac{1+Tiu}{iu(1+iu)} \quad (3.3)$$

$$u = \omega \tau_1, \quad T = \tau_2/\tau_1 = 1 + C_2/C_1 > 1$$

$$\operatorname{Re} Z^*(u) = \frac{(-1+T)^2}{T^2(1+u^2)}, \quad \operatorname{Im} Z^*(u) = -\frac{(-1+T)(1+Tu^2)}{T^2 u(1+u^2)}$$

$$\lim_{u \rightarrow 0} \operatorname{Re} Z^*(u) = \frac{(-1+T)^2}{T^2} = \frac{C_2^2}{(C_1 + C_2)^2}$$

(Fig. 3.4)

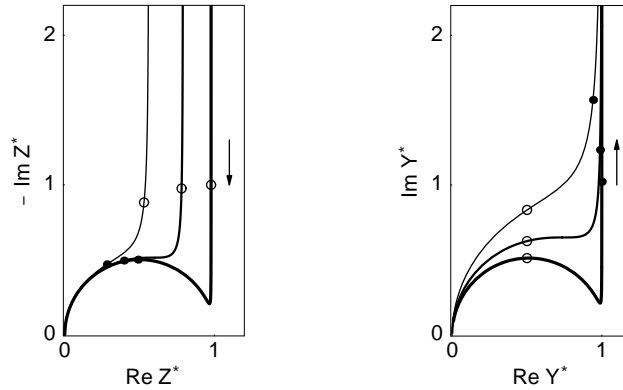


Figure 3.4: Nyquist diagram of the reduced impedance and admittance ($Y^* = R_1 Y$) for the $((R_1+C_2)/C_1)$ circuit (Fig. 3.3, Eq. (3.3)) plotted for $T = 4, 9, 90$. The line thickness increases with increasing T . Horizontal tangent is observed for $T \geq 9$. ($C_2/C_1 \geq 8$). Dots: reduced characteristic angular frequency $u_{c1} = 1$; circles: reduced characteristic angular frequency: $u_{c2} = 1/T$.

3.3 Transformation formulae between $((R/C)/C)$ and $((R+C)/C)$ circuits

3.3.1 Transformation formulae $((R/C)/C) \rightarrow ((R+C)/C)$

$$C_{22} = \frac{C_{11} C_{21}}{C_{11} + C_{21}}, \quad R_{12} = \frac{(C_{11} + C_{21})^2 R_{11}}{C_{21}^2}, \quad C_{12} = \frac{C_{21}^2}{C_{11} + C_{21}}$$

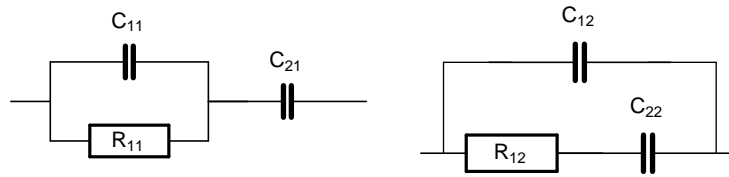


Figure 3.5: The $((R/C)/C)$ and $((R+C)/C)$ circuits are non-distinguishable [3, 2, 1, 6].

3.3.2 Transformation formulae $((R+C)/C) \rightarrow ((R/C)/C)$

$$C_{11} = C_{22} + \frac{C_{22}^2}{C_{12}}, R_{11} = \frac{C_{12}^2 R_{12}}{(C_{12} + C_{22})^2}, C_{21} = C_{12} + C_{22}$$

Chapter 4

Circuits made of two Rs and two Cs

4.1 Circuit $((R_1/C_1)+(R_2/C_2))$

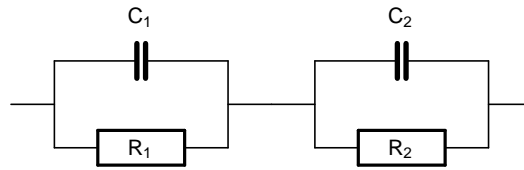


Figure 4.1: Circuit $((R_1/C_1)+(R_2/C_2))$.

4.1.1 Impedance

$$Z(\omega) = \frac{1}{i\omega C_1 + \frac{1}{R_1}} + \frac{1}{i\omega C_2 + \frac{1}{R_2}} = \frac{(R_1 + R_2)(1 + i\omega\tau_3)}{(1 + i\omega\tau_1)(1 + i\omega\tau_2)}$$

$$\tau_1 = R_1 C_1, \tau_2 = R_2 C_2, \tau_3 = \frac{(C_1 + C_2) R_1 R_2}{R_1 + R_2} = \frac{\tau_1 R_2 + \tau_2 R_1}{R_1 + R_2}$$

$$\operatorname{Re} Z(\omega) = \frac{(R_1 + R_2)(1 + \omega^2(-\tau_1\tau_2 + (\tau_1 + \tau_2)\tau_3))}{(1 + \omega^2\tau_1^2)(1 + \omega^2\tau_2^2)}$$

$$\operatorname{Im} Z(\omega) = -\frac{\omega(R_1 + R_2)(\tau_1 + \tau_2 + (-1 + \omega^2\tau_1\tau_2)\tau_3)}{(1 + \omega^2\tau_1^2)(1 + \omega^2\tau_2^2)}$$

4.1.2 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R_1 + R_2} = \frac{1 + \rho + (T + \rho)iu}{(1 + \rho)(1 + iu)(1 + iT)}$$

$$u = R_2 C_2 \omega, \rho = R_1/R_2, T = R_1 C_1/(R_2 C_2) = \gamma\rho, \gamma = C_1/C_2$$

(Figs. 4.2-4.5)

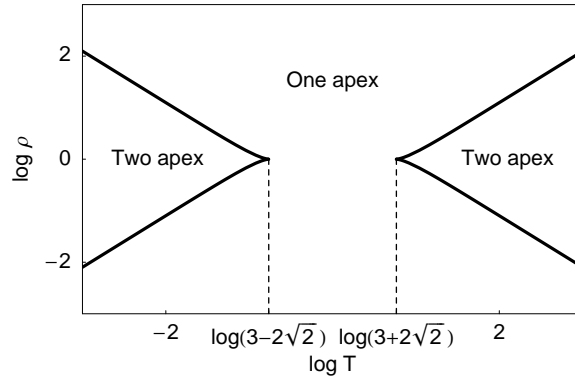


Figure 4.2: Case diagram for the $((R_1/C_1)+(R_2/C_2))$ circuit plotted using the $\log \rho$ vs. $\log T$ representation.

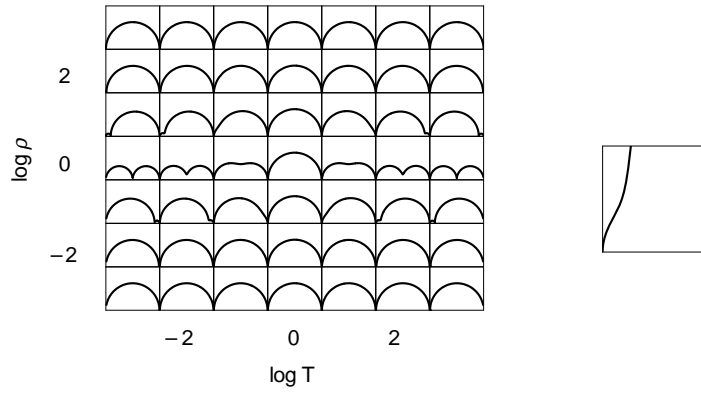


Figure 4.3: Array of impedance diagrams plotted for the $((R_1/C_1)+(R_2/C_2))$ circuit, depending on ρ and T values, and enlargement of the high frequency part of the diagram calculated for $T = 10^{-2}$ and $\rho = 10^{-2}$.

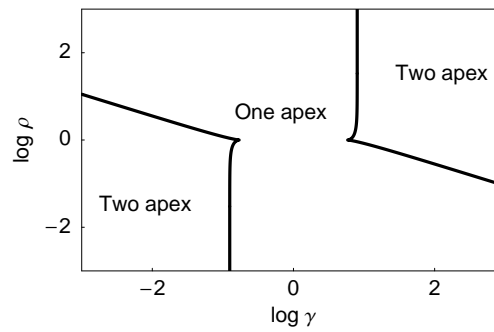


Figure 4.4: Case diagram for the $((R_1/C_1)+(R_2/C_2))$ circuit, using the $\log \rho$ vs. $\log \gamma$ representation.

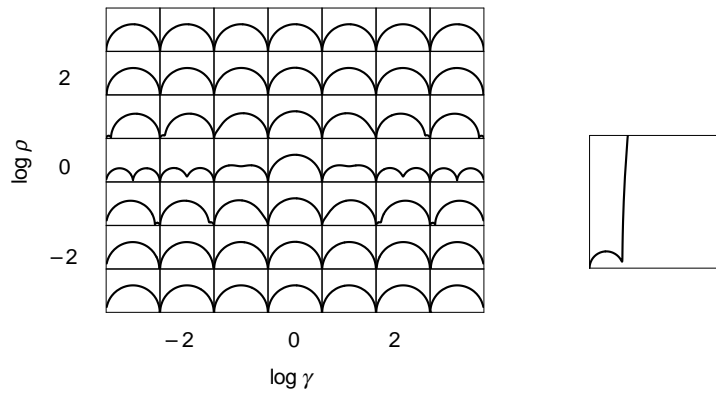
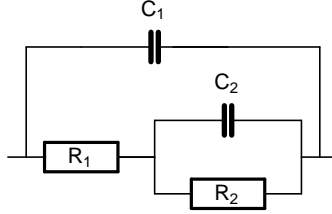


Figure 4.5: Array of impedance diagrams plotted for the $((R_1/C_1)+(R_2/C_2))$ circuit, depending on ρ and γ values and enlargement of the high frequency part of the diagram calculated for $\gamma = 10^{-2}$ and $\rho = 10^{-2}$.

4.2 Circuit $((R_1 + (R_2/C_2))/C_1)$

Figure 4.6: Circuit $((R_1 + (R_2/C_2))/C_1)$.

4.2.1 Impedance

$$Z(\omega) = \frac{1}{i\omega C_1 + \frac{1}{R_1 + \frac{R_2}{1 + i\omega C_2 R_2}}}$$

$$Z(\omega) = \frac{(R_1 + R_2) \left(1 + \frac{i\omega C_2 R_1 R_2}{R_1 + R_2}\right)}{1 + i\omega (C_2 R_2 + C_1 (R_1 + R_2)) + (i\omega)^2 C_1 C_2 R_1 R_2}$$

$$Z(\omega) = \frac{(R_1 + R_2) (1 + i\omega \tau_3)}{(1 + i\omega \tau_1) (1 + i\omega \tau_2)}, \quad \tau_3 = \frac{C_2 R_1 R_2}{R_1 + R_2}$$

The poles of the impedance of a circuit made of Rs and Cs are always real [5].

$$\tau_1 = \frac{C_2 R_2 + C_1 (R_1 + R_2) - \sqrt{-4 C_1 C_2 R_1 R_2 + (C_2 R_2 + C_1 (R_1 + R_2))^2}}{2} \quad (4.1)$$

$$\tau_2 = \frac{C_2 R_2 + C_1 (R_1 + R_2) + \sqrt{-4 C_1 C_2 R_1 R_2 + (C_2 R_2 + C_1 (R_1 + R_2))^2}}{2} \quad (4.2)$$

4.2.2 Reduced impedance

$$Z^*(u) = \frac{Z(u)}{R_1 + R_2} = \frac{\rho}{1 + \rho} \frac{1 + \rho(1 + iu)}{iuT + \rho(1 + iu)(1 + iuT)}$$

$$u = R_2 C_2 \omega, \quad \rho = R_1/R_2, \quad T = R_1 C_1/(R_2 C_2) = \gamma \rho, \quad \gamma = C_1/C_2$$

(Figs. 4.7-4.10)

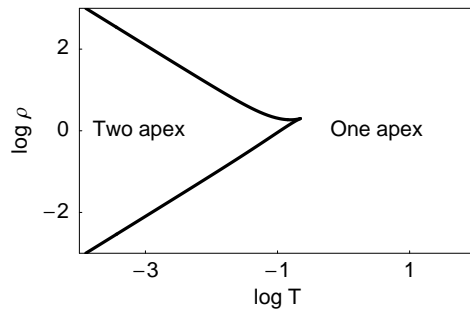


Figure 4.7: Case diagram for the $((R_1+(R_2/C_2))/C_1)$ circuit plotted using the $\log \rho$ vs. $\log T$ representation.

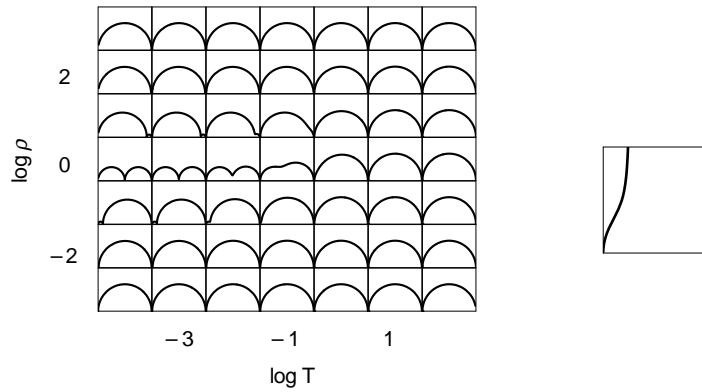


Figure 4.8: Array of impedance diagrams plotted for the $((R_1+(R_2/C_2))/C_1)$ circuit, depending on ρ and T values, and enlargement of the high frequency part of the diagram calculated for $T = 10^{-3}$ and $\rho = 10^{-3}$.

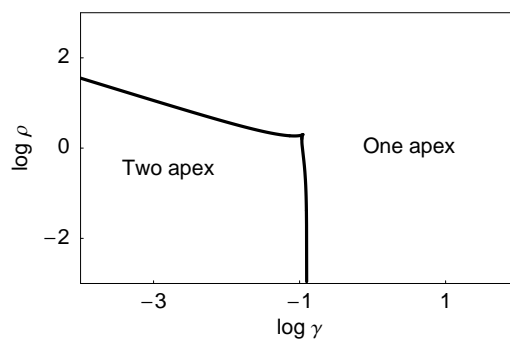


Figure 4.9: Case diagram for the $((R_1+(R_2/C_2))/C_1)$ circuit plotted using the $\log \rho$ vs. $\log \gamma$ representation.

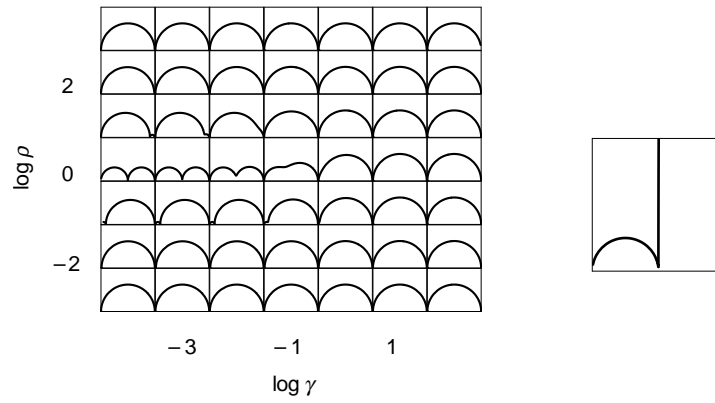
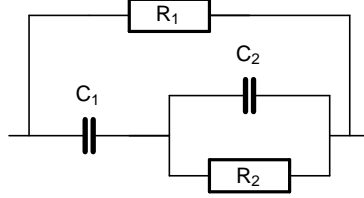


Figure 4.10: Array of impedance diagrams plotted for the $((R_1 + (R_2/C_2))/C_1)$ circuit, depending on ρ and γ values, and enlargement of the high frequency part of the diagram calculated for $\gamma = 10^{-3}$ and $\rho = 10^{-3}$.

4.3 Circuit $((C_1 + (R_2/C_2))/R_1)$

Figure 4.11: Circuit $((C_1 + (R_2/C_2))/R_1)$.

4.3.1 Impedance

$$Z(\omega) = \frac{1}{\frac{1}{R_1} + \frac{1}{\frac{1}{i\omega C_1} + \frac{R_2}{1 + i\omega C_2 R_2}}}$$

$$Z(\omega) = \frac{R_1 (1 + i\omega (C_1 + C_2) R_2)}{1 + i\omega (C_2 R_2 + C_1 (R_1 + R_2)) + (i\omega)^2 C_1 C_2 R_1 R_2}$$

$$Z(\omega) = \frac{R_1 (1 + i\omega \tau_3)}{(1 + i\omega \tau_1) (1 + i\omega \tau_2)}, \quad \tau_3 = (C_1 + C_2) R_2, \quad \tau_1 : \text{Éq. (4.1)}, \quad \tau_2 : \text{Éq. (4.2)}$$

4.3.2 Reduced impedance

$$Z^*(u) = Z(u)/R_1 = \frac{\rho + iu (\rho + T)}{iuT + \rho (1 + iu) (1 + iuT)}$$

$$u = R_2 C_2 \omega, \quad \rho = R_1/R_2, \quad T = R_1 C_1 / (R_2 C_2) = \gamma \rho, \quad \gamma = C_1/C_2$$

(Figs. 4.12 and 4.13)

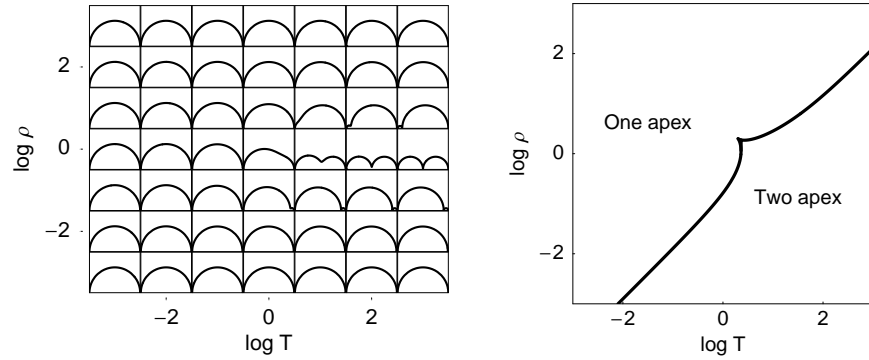


Figure 4.12: Impedance diagrams array and case diagram for the $((C_1+(R_2/C_2))/R_1)$ circuit using the $\log \rho$ vs. $\log T$ representation.

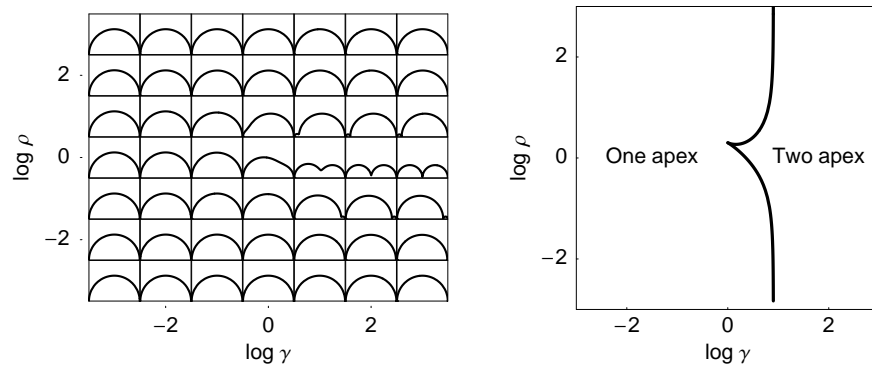
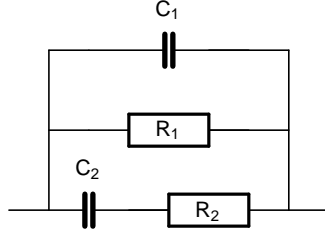


Figure 4.13: Impedance diagrams array and case diagram for the $((C_1+(R_2/C_2))/R_1)$ circuit using the $\log \rho$ vs. $\log \gamma$ representation.

4.4 Circuit $((C_2+R_2)/R_1)/C_1$

Figure 4.14: Circuit $((C_2+R_2)/R_1)/C_1$.

4.4.1 Impedance

$$Z(\omega) = \frac{1}{i\omega C_1 + \frac{1}{R_1} + \frac{1}{\frac{1}{i\omega C_2} + R_2}}$$

$$Z(\omega) = \frac{R_1 (1 + i\omega C_2 R_2)}{1 + i\omega (C_1 R_1 + C_2 (R_1 + R_2)) + (i\omega)^2 C_1 C_2 R_1 R_2}$$

$$Z(\omega) = \frac{R_1 (1 + i\omega \tau_3)}{(1 + i\omega \tau_1) (1 + i\omega \tau_2)}$$

$\tau_3 = R_2 C_2$; τ_1 : Eq. (4.1), τ_2 : Eq. (4.2) (exchanging subscripts 1 and 2)

4.4.2 Reduced impedance

$$Z^*(u) = Z(u)/R_1 = \frac{1 + iu}{1 + iu (1 + \rho + \tau (1 + iu))}$$

$$u = R_2 C_2 \omega, \rho = R_1/R_2, T = R_1 C_1/(R_2 C_2) = \gamma \rho, \gamma = C_1/C_2$$

(Figs. 4.15 and 4.16)

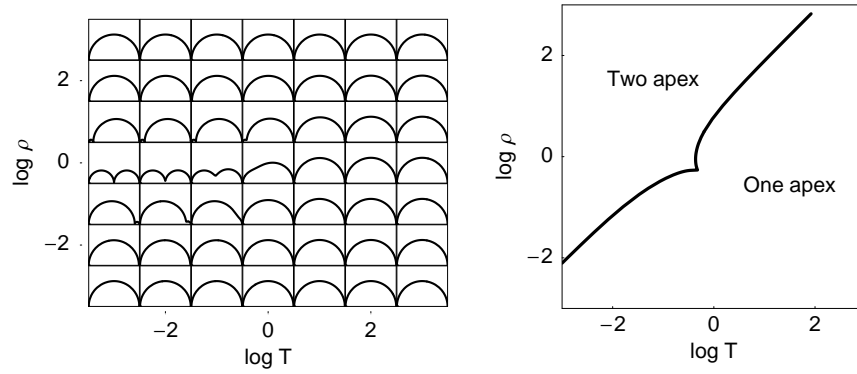


Figure 4.15: Impedance diagrams array and case diagram for the $\left(\frac{C_2+R_2}{R_1}\right)/C_1$ circuit using the $\log \rho$ vs. $\log T$ representation.

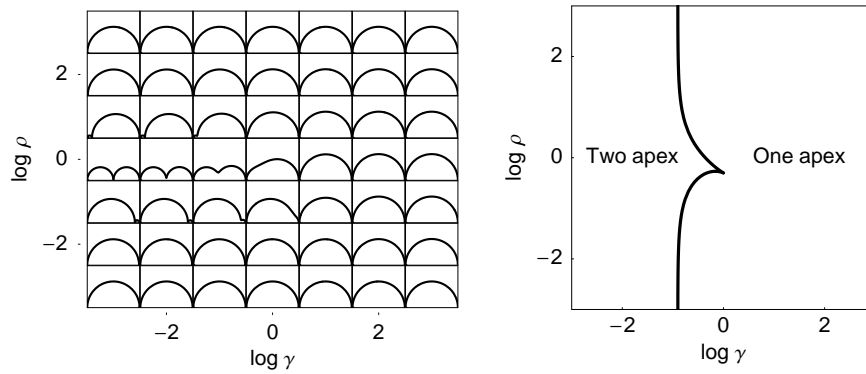


Figure 4.16: Impedance diagrams array and case diagram for the $\left(\frac{C_2+R_2}{R_1}\right)/C_1$ circuit using the $\log \rho$ vs. $\log \gamma$ representation.

4.5 Transformation formulae for the four circuits made of two Rs and two Cs

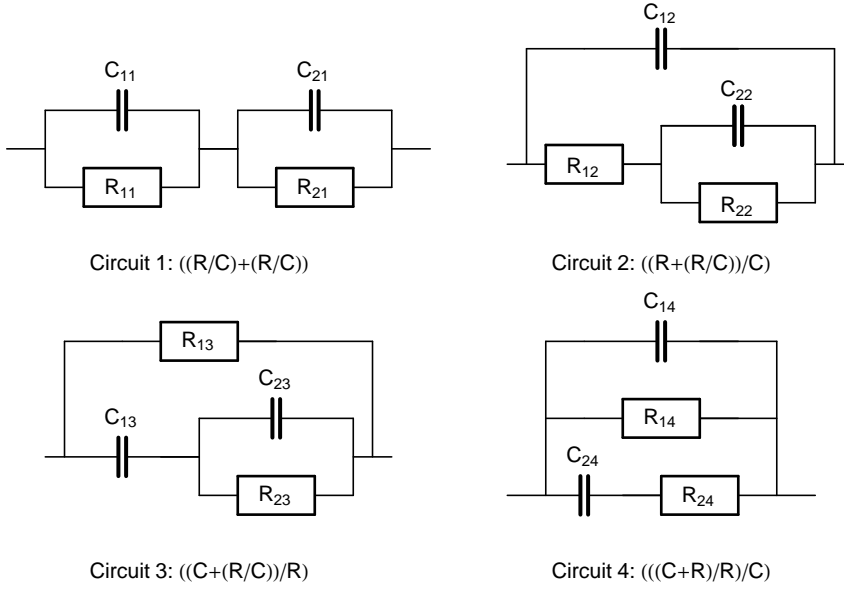


Figure 4.17: The four circuits are non-distinguishable [3, 2, 1, 6].

The four circuits are non-distinguishable [3, 2, 1, 6]. 12 transformation formulae exist between the four circuits.

4.5.1 Transformation formulae circuit 2 \rightarrow circuit 1

$$C_{11} = \frac{1}{2 C_{22} R_{22}^2} \sqrt{C_{22}^2 R_{22}^2 + 2 C_{12} C_{22} R_{22} (-R_{12} + R_{22}) + C_{12}^2 (R_{12} + R_{22})^2} \\ \times (C_{22} R_{22} - C_{12} (R_{12} + R_{22}) + \sqrt{C_{22}^2 R_{22}^2 + 2 C_{12} C_{22} R_{22} (-R_{12} + R_{22}) + C_{12}^2 (R_{12} + R_{22})^2})$$

$$C_{21} = \frac{1}{2 C_{22} R_{22}^2} \sqrt{C_{22}^2 R_{22}^2 + 2 C_{12} C_{22} R_{22} (-R_{12} + R_{22}) + C_{12}^2 (R_{12} + R_{22})^2} \\ \times (-C_{22} R_{22} + C_{12} (R_{12} + R_{22}) + \sqrt{C_{22}^2 R_{22}^2 + 2 C_{12} C_{22} R_{22} (-R_{12} + R_{22}) + C_{12}^2 (R_{12} + R_{22})^2})$$

$$R_{21} = \left(C_{22} (R_{12} - R_{22}) R_{22} - C_{12} (R_{12} + R_{22})^2 + \right. \\ \left. (R_{12} + R_{22}) \sqrt{C_{22}^2 R_{22}^2 + 2 C_{12} C_{22} R_{22} (-R_{12} + R_{22}) + C_{12}^2 (R_{12} + R_{22})^2} \right) / \\ \left(2 \sqrt{C_{22}^2 R_{22}^2 + 2 C_{12} C_{22} R_{22} (-R_{12} + R_{22}) + C_{12}^2 (R_{12} + R_{22})^2} \right)$$

$$R_{11} = \frac{1}{2} \left(R_{12} + R_{22} + \frac{C_{22} R_{22} (-R_{12} + R_{22}) + C_{12} (R_{12} + R_{22})^2}{\sqrt{C_{22}^2 R_{22}^2 + 2 C_{12} C_{22} R_{22} (-R_{12} + R_{22}) + C_{12}^2 (R_{12} + R_{22})^2}} \right)$$

4.5.2 Transformation formulae circuit 1 \rightarrow circuit 2

$$C_{12} = \frac{C_{11} C_{21}}{C_{11} + C_{21}}, C_{22} = \frac{(C_{11}^2 R_{11} + C_{21}^2 R_{21})^2}{(C_{11} + C_{21}) (C_{11} R_{11} - C_{21} R_{21})^2}$$

$$R_{12} = \frac{(C_{11} + C_{21})^2 R_{11} R_{21}}{C_{11}^2 R_{11} + C_{21}^2 R_{21}}, R_{22} = \frac{(C_{11} R_{11} - C_{21} R_{21})^2}{C_{11}^2 R_{11} + C_{21}^2 R_{21}}$$

4.5.3 Transformation formulae circuit 3 \rightarrow circuit 1

$$C_{11} = \frac{1}{2 C_{13}^2 R_{13}^2} (C_{13}^2 (C_{13} + C_{23}) R_{13}^2 + 2 C_{13} (C_{13}^2 - C_{23}^2) R_{13} R_{23} + \\ (C_{13} + C_{23})^3 R_{23}^2 - (C_{13} (C_{13} - C_{23}) R_{13} + (C_{13} + C_{23})^2 R_{23}) \\ \times \sqrt{C_{23}^2 R_{23}^2 + 2 C_{13} C_{23} R_{23} (-R_{13} + R_{23}) + C_{13}^2 (R_{13} + R_{23})^2})$$

$$C_{21} = \frac{1}{2 C_{13}^2 R_{13}^2} (C_{13}^2 (C_{13} + C_{23}) R_{13}^2 + 2 C_{13} (C_{13}^2 - C_{23}^2) R_{13} R_{23} + \\ (C_{13} + C_{23})^3 R_{23}^2 + (C_{13} (C_{13} - C_{23}) R_{13} + (C_{13} + C_{23})^2 R_{23}) \\ \times \sqrt{C_{23}^2 R_{23}^2 + 2 C_{13} C_{23} R_{23} (-R_{13} + R_{23}) + C_{13}^2 (R_{13} + R_{23})^2})$$

$$R_{21} = R_{13} (C_{13} R_{13} - (C_{13} + C_{23}) R_{23} + \\ \sqrt{C_{23}^2 R_{23}^2 + 2 C_{13} C_{23} R_{23} (-R_{13} + R_{23}) + C_{13}^2 (R_{13} + R_{23})^2}) / \\ \left(2 \sqrt{C_{23}^2 R_{23}^2 + 2 C_{13} C_{23} R_{23} (-R_{13} + R_{23}) + C_{13}^2 (R_{13} + R_{23})^2} \right)$$

$$R_{11} = \frac{R_{13}}{2} \left(1 + \frac{-C_{13} R_{13} + (C_{13} + C_{23}) R_{23}}{\sqrt{C_{23}^2 R_{23}^2 + 2 C_{13} C_{23} R_{23} (-R_{13} + R_{23}) + C_{13}^2 (R_{13} + R_{23})^2}} \right)$$

4.5.4 Transformation formulae circuit 1 → circuit 3

$$R_{13} = R_{11} + R_{21}, C_{23} = \frac{C_{11} C_{21} (C_{11} R_{11}^2 + C_{21} R_{21}^2)}{(C_{11} R_{11} - C_{21} R_{21})^2}$$

$$C_{13} = \frac{C_{11} R_{11}^2 + C_{21} R_{21}^2}{(R_{11} + R_{21})^2}, R_{23} = \frac{R_{11} R_{21} (R_{11} + R_{21}) (C_{11} R_{11} - C_{21} R_{21})^2}{(C_{11} R_{11}^2 + C_{21} R_{21}^2)^2}$$

4.5.5 Transformation formulae circuit 4 → circuit 1

$$C_{11} = \frac{1}{2 C_{24} R_{14}^2} \sqrt{C_{14}^2 R_{14}^2 + 2 C_{14} C_{24} R_{14} (R_{14} - R_{24}) + C_{24}^2 (R_{14} + R_{24})^2}$$

$$\times (C_{14} R_{14} - C_{24} (R_{14} + R_{24}) + \sqrt{C_{14}^2 R_{14}^2 + 2 C_{14} C_{24} R_{14} (R_{14} - R_{24}) + C_{24}^2 (R_{14} + R_{24})^2})$$

$$C_{21} = \frac{1}{2 C_{24} R_{14}^2} \sqrt{C_{14}^2 R_{14}^2 + 2 C_{14} C_{24} R_{14} (R_{14} - R_{24}) + C_{24}^2 (R_{14} + R_{24})^2}$$

$$\times (-C_{14} R_{14} + C_{24} (R_{14} + R_{24}) + \sqrt{C_{14}^2 R_{14}^2 + 2 C_{14} C_{24} R_{14} (R_{14} - R_{24}) + C_{24}^2 (R_{14} + R_{24})^2})$$

$$R_{21} = (R_{14} ((C_{14} + C_{24}) R_{14} - C_{24} R_{24} + \sqrt{C_{14}^2 R_{14}^2 + 2 C_{14} C_{24} R_{14} (R_{14} - R_{24}) + C_{24}^2 (R_{14} + R_{24})^2})) /$$

$$\left(2 \sqrt{C_{14}^2 R_{14}^2 + 2 C_{14} C_{24} R_{14} (R_{14} - R_{24}) + C_{24}^2 (R_{14} + R_{24})^2} \right)$$

$$R_{11} = \frac{R_{14}}{2} \left(1 + \frac{-(C_{14} + C_{24}) R_{14} + C_{24} R_{24}}{\sqrt{C_{14}^2 R_{14}^2 + 2 C_{14} C_{24} R_{14} (R_{14} - R_{24}) + C_{24}^2 (R_{14} + R_{24})^2}} \right)$$

4.5.6 Transformation formulae circuit 1 → circuit 4

$$C_{14} = \frac{C_{11} C_{21}}{C_{11} + C_{21}}, R_{14} = R_{11} + R_{21}$$

$$R_{24} = \frac{(C_{11} + C_{21})^2 R_{11} R_{21} (R_{11} + R_{21})}{(C_{11} R_{11} - C_{21} R_{21})^2}, C_{24} = \frac{(C_{11} R_{11} - C_{21} R_{21})^2}{(C_{11} + C_{21}) (R_{11} + R_{21})^2}$$

4.5.7 Transformation formulae circuit 3 → circuit 2

$$C_{12} = \frac{C_{13} C_{23}}{C_{13} + C_{23}}, C_{22} = \frac{(C_{13}^2 R_{13} + (C_{13} + C_{23})^2 R_{23})^2}{C_{13}^2 (C_{13} + C_{23}) R_{13}^2}$$

$$R_{12} = \frac{(C_{13} + C_{23})^2 R_{13} R_{23}}{C_{13}^2 R_{13} + (C_{13} + C_{23})^2 R_{23}}, R_{22} = \frac{C_{13}^2 R_{13}^2}{C_{13}^2 R_{13} + (C_{13} + C_{23})^2 R_{23}}$$

4.5.8 Transformation formulae circuit 2 \rightarrow circuit 3

$$R_{13} = R_{12} + R_{22}, C_{23} = \frac{C_{12} \left(C_{22} R_{22}^2 + C_{12} (R_{12} + R_{22})^2 \right)}{C_{22} R_{22}^2}$$

$$C_{13} = C_{12} + \frac{C_{22} R_{22}^2}{(R_{12} + R_{22})^2}, R_{23} = \frac{C_{22}^2 R_{12} R_{22}^3 (R_{12} + R_{22})}{\left(C_{22} R_{22}^2 + C_{12} (R_{12} + R_{22})^2 \right)^2}$$

4.5.9 Transformation formulae circuit 4 \rightarrow circuit 2

$$C_{12} = C_{14}, C_{22} = \frac{C_{24} (R_{14} + R_{24})^2}{R_{14}^2}, R_{12} = \frac{R_{14} R_{24}}{R_{14} + R_{24}}, R_{22} = \frac{R_{14}^2}{R_{14} + R_{24}}$$

4.5.10 Transformation formulae circuit 2 \rightarrow circuit 4

$$C_{14} = C_{12}, R_{14} = R_{12} + R_{22}, R_{24} = R_{12} + \frac{R_{12}^2}{R_{22}}, C_{24} = \frac{C_{22} R_{22}^2}{(R_{12} + R_{22})^2}$$

4.5.11 Transformation formulae circuit 4 \rightarrow circuit 3

$$R_{13} = R_{14}, C_{23} = C_{14} + \frac{C_{14}^2}{C_{24}}, C_{13} = C_{14} + C_{24}, R_{23} = \frac{C_{24}^2 R_{24}}{(C_{14} + C_{24})^2}$$

4.5.12 Transformation formulae circuit 3 \rightarrow circuit 4

$$C_{14} = \frac{C_{13} C_{23}}{C_{13} + C_{23}}, R_{24} = \frac{(C_{13} + C_{23})^2 R_{23}}{C_{13}^2}, R_{14} = R_{13}, C_{24} = \frac{C_{13}^2}{C_{13} + C_{23}}$$

Bibliography

- [1] FLETCHER, S. *J. Electrochem. Soc.* 141 (1994), 1823.
- [2] MACDONALD, J. R. *Impedance spectroscopy. Emphasizing solid materials and systems.* John Wiley & Sons, 1987.
- [3] NOVOSEL'SKII, I. M., GUDINA, N. N., AND FETISTOV, Y. I. *Élektrokimiya* 8 (1972), 565.
- [4] SIBERT, E. *Electrosorption sur surface Pt(111), influence des anions.* PhD thesis, ENSEEG/INPG, Grenoble, Sept. 2000.
- [5] TEMES, G. C., AND LAPATRA, J. W. *Introduction to Circuits Synthesis and Design.* McGraw-Hill, New-York, 1977.
- [6] WALTER, E., AND PRONZATO, L. *Identification de modèles paramétriques à partir de données expérimentales.* Masson, Paris, 1994.